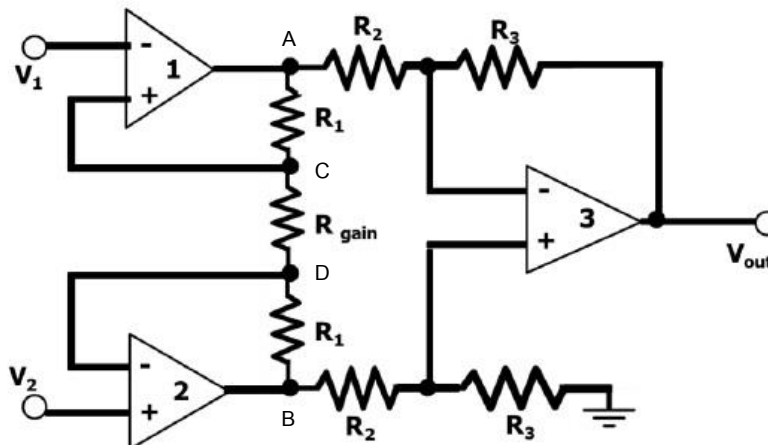


Time: 10:00-11:30 h.  
Marks: 100

Open Book

Attempt all questions.

- Q.1** An instrumentation amplifier is used to amplify very low-level signals, rejecting noise and interference signals. A circuit of the instrumentation amplifier is shown below using 3 op-amps.
- (a) Determine the output voltage,  $V_{out}$ , as a function of the difference of the input voltage,  $V_2 - V_1$ .
- (b) Determine the amplifying gain when all the resistors are selected as 10 k $\Omega$ . (25)



**Solution**

(a)

The circuit of op-amp 3 is differential amplifier, thus.

$$V_{out} = \frac{R_3}{R_2}(V_B - V_A)$$

The voltage at both inputs of op-amp 1 and op-amp 2 must be the same, thus

$$V_C = V_1$$

$$V_D = V_2$$

The current,  $I$ , flowing between B through D through C and A is the same current, thus

$$V_D - V_C = V_2 - V_1 = IR_{gain}$$

$$I = \frac{V_2 - V_1}{R_{gain}}$$

$$V_B - V_A = I(2R_1 + R_{gain}) = \frac{V_2 - V_1}{R_{gain}}(2R_1 + R_{gain})$$

Substitute the last equation into the first equation,

$$V_{out} = \frac{R_3}{R_2} \left( \frac{V_2 - V_1}{R_{gain}} (2R_1 + R_{gain}) \right) = \frac{R_3(2R_1 + R_{gain})}{R_2 R_{gain}} (V_2 - V_1)$$


(b) When all the resistors are 10 kΩ, the amplifying gain becomes

$$\frac{V_{out}}{V_2 - V_1} = \frac{10(20 + 10)}{10(10)} = 3$$

**Q.2** A passive notch filter has the circuit as shown below.

(a) Determine the transfer function from the input voltage,  $V_{in}$ , to the output voltage,  $V_{out}$ , and the notch frequency (in rad/s),  $\omega_n$ , whose the output voltage becomes zero.

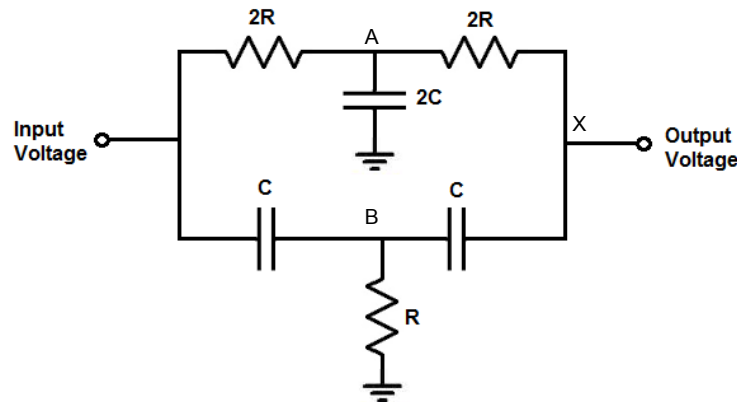(b) If  $R = 10 \text{ k}\Omega$  is selected, determine value of  $C$  that eliminates the input signal at 50 Hz completely. (25)



**Solution**

(a)

At node A,

$$\frac{V_{in} - V_A}{2R} + \frac{V_{out} - V_A}{2R} - 2CsV_A = 0$$

$$\frac{V_{in}}{2R} + \frac{V_{out}}{2R} = \frac{(1 + 2RCs)}{R} V_A$$

$$\frac{V_{in}}{2(1 + 2RCs)} + \frac{V_{out}}{2(1 + 2RCs)} = V_A$$

At node B,

$$(V_{in} - V_B)Cs + (V_{out} - V_B)Cs - \frac{V_B}{R} = 0$$

$$V_{in}Cs + V_{out}Cs = \frac{(1 + 2RCs)}{R}V_B$$

$$\frac{RCsV_{in}}{(1 + 2RCs)} + \frac{RCsV_{out}}{(1 + 2RCs)} = V_B$$

At node X,

$$\frac{V_{out} - V_A}{2R} + (V_{out} - V_B)Cs = 0$$

$$\frac{V_{out}}{2R} + V_{out}Cs = \frac{V_A}{2R} + V_BCs$$

$$\left(\frac{1 + 2RCs}{2RCs}\right)V_{out} - \frac{V_A}{2RCs} = V_B$$

Equate  $V_B$ ,

$$\begin{aligned} \frac{RCsV_{in}}{(1 + 2RCs)} + \frac{RCsV_{out}}{(1 + 2RCs)} &= \left(\frac{1 + 2RCs}{2RCs}\right)V_{out} - \frac{V_A}{2RCs} \\ -\left(\frac{2(RCs)^2}{(1 + 2RCs)}V_{in} + \frac{2(RCs)^2 - (1 + 2RCs)^2}{(1 + 2RCs)}V_{out}\right) &= V_A \end{aligned}$$

Equate  $V_A$ ,

$$\begin{aligned} \frac{1}{2(1 + 2RCs)}V_{in} + \frac{1}{2(1 + 2RCs)}V_{out} &= -\frac{2(RCs)^2}{(1 + 2RCs)}V_{in} - \frac{2(RCs)^2 - (1 + 2RCs)^2}{(1 + 2RCs)}V_{out} \\ \frac{1 + 4(RCs)^2 + 2(1 + 2RCs)^2}{2(1 + 2RCs)}V_{out} &= -\frac{1 + 4(RCs)^2}{2(1 + 2RCs)}V_{in} \\ \frac{V_{out}}{V_{in}} = G(s) &= -\frac{1 + 4(RCs)^2}{1 + 4(RCs)^2 + 2(1 + 2RCs)^2} = -\frac{1 + 4R^2C^2s^2}{3 + 8RCs + 12R^2C^2s^2} \end{aligned}$$

Substitute  $s = \omega j$ ,

$$G(\omega j) = -\frac{1 - 4R^2C^2\omega^2}{3 - 12R^2C^2\omega^2 + 8RC\omega j}$$

Thus,

$$\omega_n = \frac{1}{2RC}$$


(b)

$$f_n = \frac{1}{4\pi RC}$$

$$50 = \frac{1}{40,000\pi C}$$

$$C = 159.2nF$$

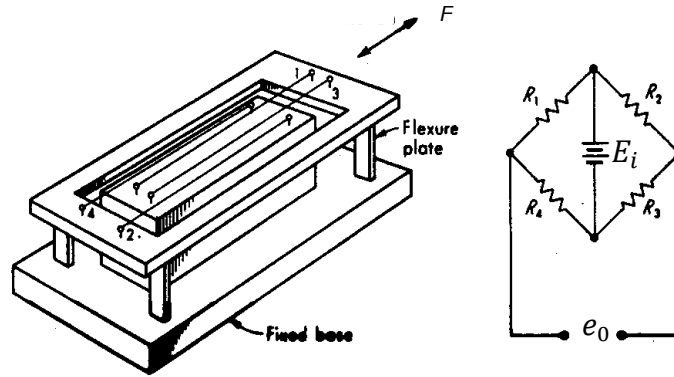**Q.3** 4 identical unbonded strain-gages; each with gage factor,  $S_g$ , of 2, nominal length,  $L$ , of 10 mm, are used to determine the distance,  $\Delta L$ , resulting from the force,  $F$ , applied to the upper plate as shown below. Determine the distance when the output reading,  $e_0$ , from the DC Wheatstone bridge circuit indicates 20 mV when the supplied voltage,  $E_i$ , is 5 V. Assume that nonlinearity of the bridge circuit is negligible. (25)



**Solution**

The voltage output from DC Wheatstone bridge circuit is determined from

$$e_0 = \frac{r}{(1+r)^2} \left[ \frac{\Delta R_1}{R_1} - \frac{\Delta R_2}{R_2} + \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4} \right] E_i = \frac{\Delta R}{R} E_i = S_g \varepsilon E_i = S_g \frac{\Delta L}{L} E_i$$

$$20 = 2 \frac{\Delta L}{10} 5000$$

$$\Delta L = 0.02 \text{ mm}$$

**Q.4** 3-axis identical accelerometer is used to determine attitude (roll ( $\theta$ ), and pitch ( $\alpha$ )) of a robot body by measuring the gravitational acceleration. When roll axis of the robot is aligned with y axis of the accelerometer and pointing to the front direction of the robot, pitch axis is aligned with x axis and pointing to the right, and yaw axis is aligned with z axis and pointing up. When the robot rolls 30 degrees then pitch -90 degrees, the output voltages from x, y, and z axes of the accelerometer become 1 V, 1.732 V, and 0 V respectively. Determine the roll angle then the pitch angle of the robot if the output voltages show -1.732 V, -0.7071 V, and -0.7071 V respectively. (25)

**Solution**

The gravitational acceleration detected from the accelerometer depends on the roll angle ( $\theta$ ), and pitch angle ( $\alpha$ ) of the robot body.

$$a_x = g \sin(\theta)$$

$$a_y = -g\cos(\theta)\sin(\alpha)$$

$$a_z = -g\cos(\theta)\cos(\alpha)$$

When the accelerometer has the sensitivity of  $K$ , the output voltages become

$$V_x = Kgsin(\theta)$$

$$V_y = -Kg\cos(\theta)\sin(\alpha)$$

$$V_z = -Kg\cos(\theta)\cos(\alpha)$$

When the robot rolls 30 degrees then pitch -90 degrees,

$$1 = Kgsin(30^\circ)$$

$$1.732 = -Kg\cos(30^\circ)\sin(-90^\circ)$$

$$0 = -Kg\cos(30^\circ)\cos(-90^\circ)$$

Thus,

$$Kg = 2$$

If the output voltages show -1.732 V, -0.7071 V, and -0.7071 V,

$$-1.732 = 2sin(\theta)$$

$$-0.7071 = -2cos(\theta)\sin(\alpha)$$

$$-0.7071 = -2cos(\theta)\cos(\alpha)$$

Thus,

$$\theta = -60^\circ$$

$$\alpha = 45^\circ$$