

**Midterm Examination Sensing and Actuation AT74.03 February 29, 2024**

Time: 10:00-11:30 h.  
Marks: 100

Open Book

Attempt all questions.

**Q.1** The frequency of the output voltage,  $V$  (in V), from a pressure sensor varies with the input pressure,  $P$  (in Bar), as expressed by


$$V = 0.1\sin((8P + 200)t)$$

When the the input pressure varies between 0-100 Bar. Design a signal conditioning that convert the pressure value (0-100 Bar) to the DC voltage,  $V_{dc}$  (0-5 V). The low-pass filter, if needed, has the cut-off frequency (3 dB attenuation) at 50 rad/s. (25)


**Solution**

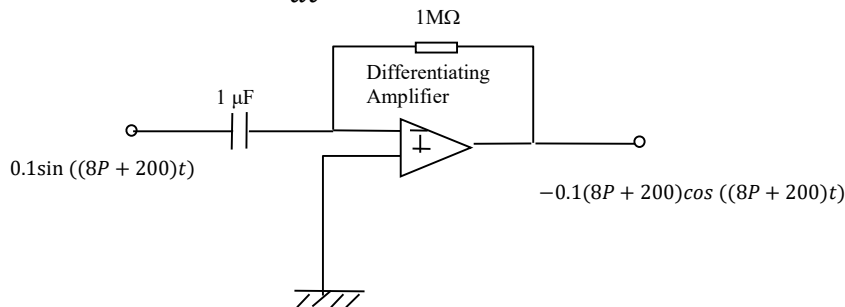1. A differentiating circuit is used to differentiate the signal so that the amplitude of the signal is a function of the input pressure.

$$\frac{dV}{dt} = 0.1(8P + 200)\cos((8P + 200)t)$$



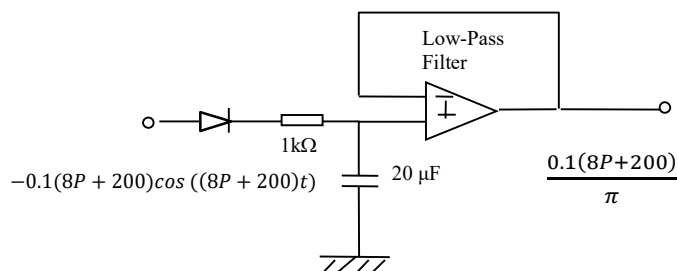2. A half-wave rectifier and a low pass filter is used to convert ac signal to dc signal.



Select a low-pass first-order filter with cut-off frequency (3db attenuation) at 50 rad/s.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

Select  $R = 1 \text{ k}\Omega$ ,

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (1000 \times 50C)^2}}$$

$$C = 20 \mu\text{F}$$

The magnitude of the dc signal from half-wave rectifier and low pass filter is considered from

$$V_{av} = \frac{\int_{\pi/2}^{3\pi/2} -0.1(8P + 200)\cos(\theta)d\theta}{2\pi} = \frac{-0.1(8P + 200)\sin(\theta)\big|_{\pi/2}^{3\pi/2}}{2\pi} = \frac{0.1(8P + 200)}{\pi}$$

At 0 Bar,

$$V_{av} = \frac{20}{\pi} = 6.37V$$

At 100 Bar,

$$V_{av} = \frac{100}{\pi} = 31.83V$$

3. Differential amplifier circuit or summing circuit is used to convert dc (6.37 - 31.83 V) to (0-5 V)


The required gain is determined.

$$G = \frac{\text{Change of output}}{\text{Change of input}} = \frac{5}{(31.83 - 6.37)} = 0.2$$


$$\frac{R_f}{R_1} = \frac{R_3}{R_2} = 0.2$$

Select  $R_1 = R_2 = 1k\Omega$ ,  $R_f = R_3 = 200\Omega$ .

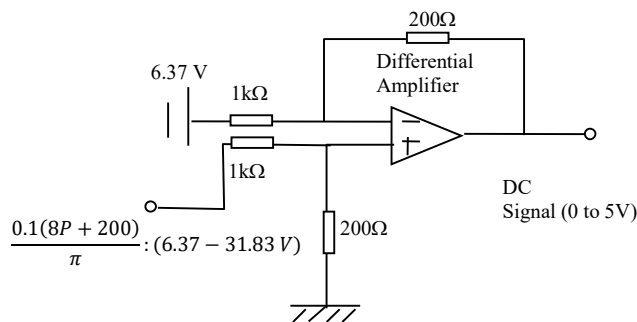
A constant voltage of 6.37 V is provided to the inverting input pin.



Thus, the whole circuit is as follows.

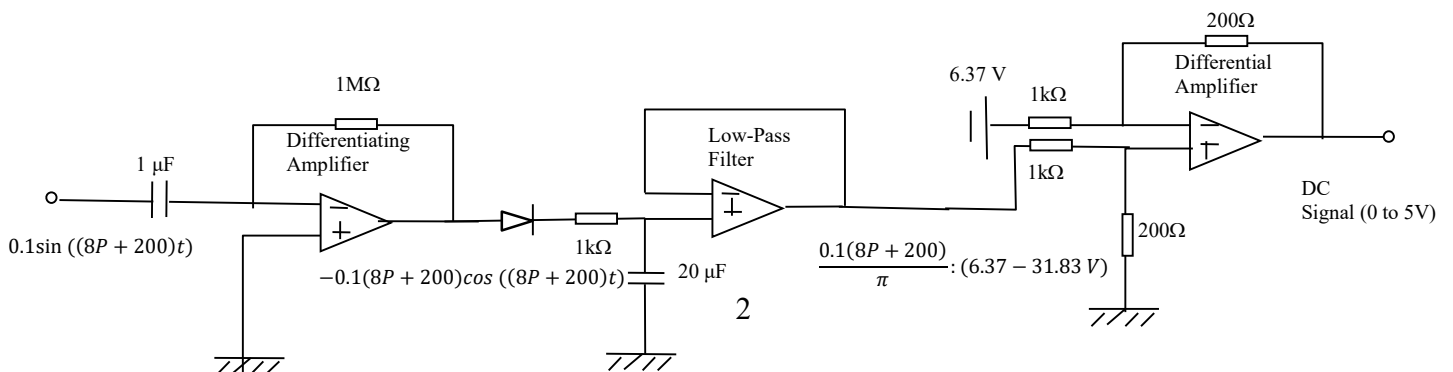

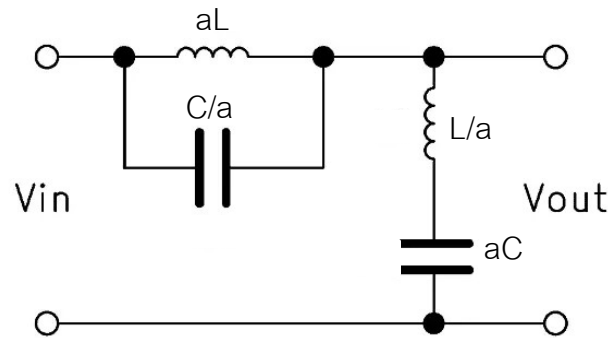**Q.2** Consider the band-stop filter circuit below. Determine the center of the rejected frequency and the 3 db rejection bandwidth when  $L = 4$  H,  $C = 100$   $\mu$ F,  $a = 10$ . (25)



**Solution**

$$\frac{V_{out}}{V_{in}} = \frac{\frac{LCs^2+1}{saC}}{\frac{LCs^2+1}{saC} + \frac{aLs}{LC^2+1}} = \frac{(LCs^2 + 1)^2}{(LCs^2 + 1)^2 + LCa^2s^2}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{(1 - LC\omega^2)^2}{(1 - LC\omega^2)^2 - LCa^2\omega^2} \right|$$

The center of the rejected frequency is obtained when the magnitude ratio becomes 0.

$$1 - LC\omega^2 = 0$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times 100 \times 10^{-6}}} = \frac{1}{\sqrt{0.0004}} = 50 \text{ rad/s} \quad (1)$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{(1 - 0.0004\omega^2)^2}{(1 - 0.0004\omega^2)^2 - 0.04\omega^2} \right| = \frac{1}{\sqrt{2}}$$

Consider

$$\frac{(1 - 0.0004\omega^2)^2}{(1 - 0.0004\omega^2)^2 - 0.04\omega^2} = \frac{1}{\sqrt{2}}$$

$$\omega^2 = -0.0001 \times 10^5, -5.9854 \times 10^5$$

Which is not possible.

Consider

$$\frac{(1 - 0.0004\omega^2)^2}{(1 - 0.0004\omega^2)^2 - 0.04\omega^2} = -\frac{1}{\sqrt{2}}$$

$$\omega^2 = 0.0006 \times 10^5, 1.0850 \times 10^5$$

$$\omega = 7.5899, 329.3870$$

Thus, 3 db rejection bandwidth

$$BW = 329.3870 - 7.5899 = 321.7971 \text{ rad/s} \quad (2)$$

**Q.3** An accelerometer and a rate gyro are used to measure the acceleration and angular velocity respectively. When the acceleration is  $1g$ , the output from the accelerometer shows  $2 V$ . When the angular velocity is  $\pi/8000$  rad/s, the output from the rate gyro shows  $0.5 V$ . Determine the outputs from the accelerometer and the rate gyro when they are located on an orbiting satellite at the height of  $100$  km from the earth surface to measure the gravitational acceleration and angular velocity of the satellite. Determine a period of an orbit of the satellite. Use the earth radius of  $6,371$  km and  $1g$  of  $9.8$  m/s<sup>2</sup>. (25)

**Solution**

Gravitational acceleration is determined from

$$g = \frac{GM}{r^2}$$

At the earth surface

$$g_0 = \frac{GM}{6,371,000^2}$$

At the height of  $100$  km above the earth surface

$$g_{100} = \frac{GM}{6,471,000^2} = 0.9693g_0$$

If the satellite is stationary, the output voltage from the accelerometer

$$V_{accel_{100}} = 0.9693V_{accel_0} = 0.9693(2) = 1.9387 V$$

However, the output voltage from the accelerometer on an orbiting satellite

$$V_{accel_{100}} = 0 V \tag{1}$$

The relation of the centrifugal force,

$$mg = m\omega^2 r$$

At the height of  $100$  km above the earth surface

$$g_{100} = 0.9693(9.8) = \omega^2(6,471,000)$$

Thus

$$\omega = 0.0012 \text{ rad/s}$$

Thus, the output voltage from the rate gyro

$$V_{rategyro_{100}} = 0.0012(0.5) / \left(\frac{\pi}{8000}\right) = 1.5279 V \tag{2}$$

The satellite period,

$$T_{100} = \frac{2\pi}{0.0012} = 5,236.0 \text{ seconds} = 87.2665 \text{ minutes} \tag{3}$$

**Q.4** An axial force is applied on a steel rectangle block with the cross section area of  $1 \text{ cm}^2$  and the length of  $10 \text{ cm}$ . Young's modulus of steel is  $200 \text{ GPa}$ . Determine the axial elastic stiffness of this block. If the force of  $10,000 \text{ N}$  is applied, determine the change of the length of the block. Then determine the voltage output from the DC Wheatstone bridge circuit, if a strain gage of  $350 \Omega$  nominal resistance and gage factor of  $2$  is used to measure the axial strain, the remaining three resistors in the bridge circuit have a constant resistance of  $350 \Omega$  each, and the supplied voltage is  $5 \text{ V}$ . (25)

**Solution**

$$E = \frac{\sigma}{\varepsilon} = \frac{FL}{A\Delta L} = \frac{kL}{A}$$

$$k = \frac{EA}{L} = \frac{(200 \times 10^9)(1 \times 10^{-4})}{(10 \times 10^{-2})} = 2 \times 10^8 \text{ N/m} \quad (1)$$

$$\Delta L = \frac{F}{k} = \frac{(1 \times 10^4)}{(2 \times 10^8)} = 5 \times 10^{-5} \text{ m} = 50 \mu\text{m} \quad (2)$$

$$V = \frac{r}{(1+r)^2} \frac{\Delta R}{R} E = \frac{r}{(1+r)^2} \frac{\Delta L}{L} SE = \frac{1}{(1+1)^2} \frac{(5 \times 10^{-5})}{(10 \times 10^{-2})} (2)(5) = 1.25 \times 10^{-3} \text{ V} = 1.25 \text{ mV} \quad (3)$$